

# Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

**Name of the participant :** S Sai Venkata Kishan Kumar

**Title of the circuit :** Ring-Counter

**Theory/Description :** A ring counter is a Shift Register (a cascade connection of flip-flops) with the output of the last flip flop connected to the input of the first. It is initialised such that only one of the flip flop output is 1 while the remainder is 0. The 1 bit is circulated so the state repeats every  $n$  clock cycles if  $n$  flip-flops are used. The "MOD" or "MODULUS" of a counter is the number of unique states. The MOD of the  $n$  flip flop ring counter is  $n$ .

Ring counters are often used in hardware design (e.g. ASCII and FPGA design) to create finite-state machines . A binary counter would require an adder circuit which is substantially more complex than a ring counter and has higher propagation delay as the number of bits increases, whereas the propagation delay of a ring counter will be nearly constant regardless of the number of bits in the code.

A general disadvantage of ring counters is that they are lower density codes than normal binary encoding of state numbers.

Straight ring counters generate fully decoded one-hot codes to that are often used to enable a specific action in each state of a cyclic control cycle.


**VHDL Code:**

```
library ieee;
use ieee.std_logic_1164.all;

entity ring_count is
port(clk : in std_logic;
     rst : in std_logic;
     op : out std_logic_vector(3 downto 0));
end entity;

architecture beh of ring_count is
signal opt : std_logic_vector(3 downto 0);
begin
process (clk,rst)
begin
if (rst = '1') then
    opt <= "1000";
elsif (clk='1') then
    opt <= opt(0) & opt(3 downto 1);
end if;
end process;
op <= opt;
end beh;
```


## Circuit Diagram(s) :

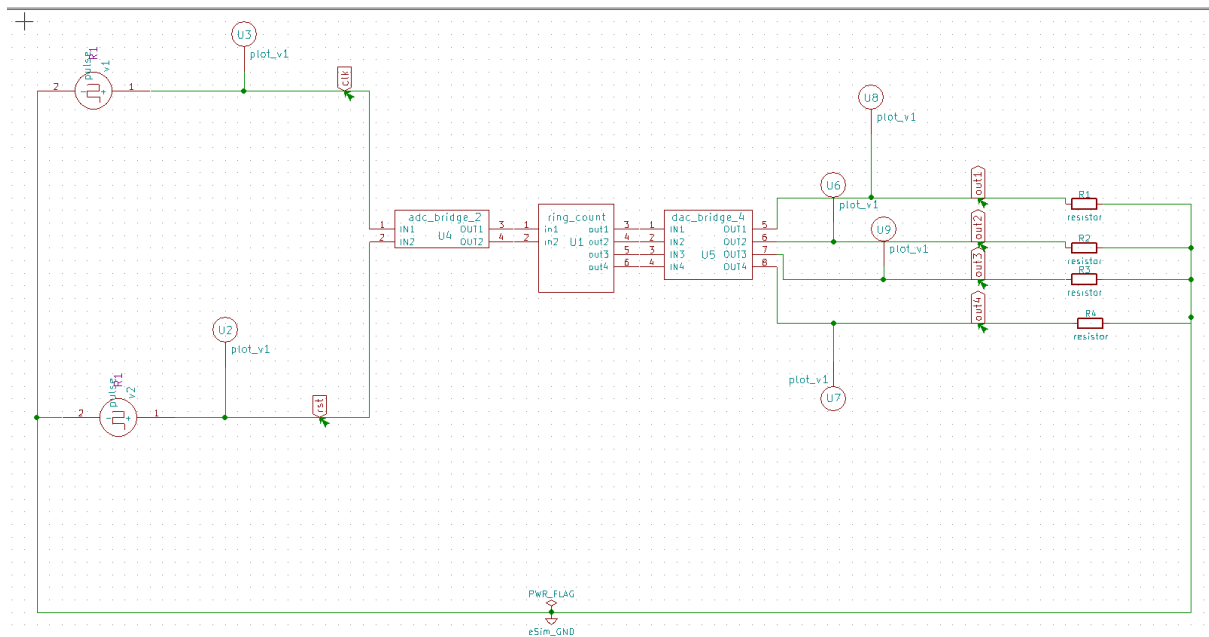


## Results (Input, Output waveforms and/or Multimeter readings) :

### NGSPICE PLOTS:-


#### 1) Plot(CLK):-

 


2) Plot(RST):-

 


3) Plot(out(3)):-

 


4) Plot(out(2)):-

 


5) Plot(out(1)):-

 


6) Plot(out(0)):-

 


    
## Python Plots:

 













 

**Table:**

<u>CLK</u>	<u>RST</u>	<u>OUT(3)</u>	<u>OUT(2)</u>	<u>OUT(1)</u>	<u>OUT(0)</u>
1	1	1	0	0	0
0	0	1	0	0	0
1	0	0	1	0	0
0	0	0	1	0	0
1	0	0	0	1	0
0	0	0	0	1	0
1	0	0	0	0	1

**Source/Reference(s) :**